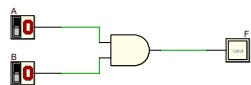


PART 1:




2 input AND gate

Logic Equation:
 $F = A \text{ and } B$

Input	Output
0 0	0
0 1	0
1 0	0
1 1	1

PART 2:

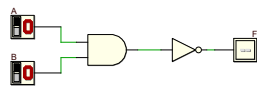


2 input NAND gate

Logic Equation:
 $F = (A \text{ and } B) \text{ not}$

Input	Output
0 0	1
0 1	1
1 0	1
1 1	0

PART 3:

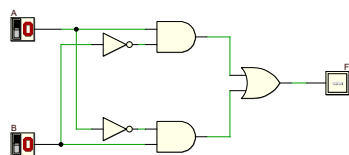

2 input XOR gate

Logic Equation:
 $F = A \text{ xor } B$
 $= (A \text{ and } B \text{ bar}) + (A \text{ bar and } B)$

Input	Output
0 0	0
0 1	1
1 0	1
1 1	0